

Digital Electronics



Principles & Applications

Seventh Edition

Roger L. Tokheim

Chapter 4

Using Logic Gates

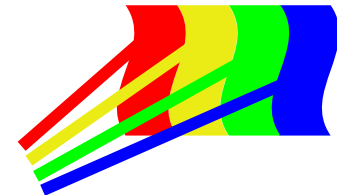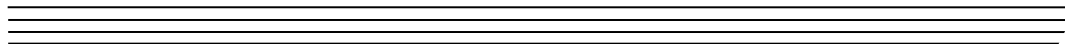

INTRODUCTION

- **Logic Circuit from a Boolean expression**
- **Minterm and maxterm Boolean expressions**
- **Boolean expression from a truth table**
- **Truth table from a Boolean expression**
- **Simplifying Boolean expressions**
- **Karnaugh mapping**


INTRODUCTION (continued)

- **Variations in Boolean expressions**
- **DeMorgan's theorem**
- **PLDs (programmable logic devices)**

“Tools of the Trade” for Solving Logic Problems

- Gate symbols
- Truth tables
- Boolean expressions

Combinational logic circuits:

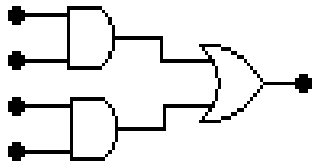


AND-OR pattern of gates

from

Sum-of-products Boolean expression such as:

$$AB + CD = Y$$

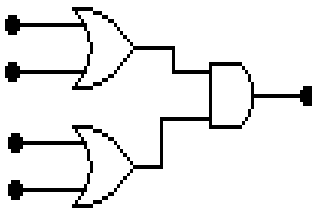

OR-AND pattern of gates

from

Product-of-sums Boolean expression such as:


$$(A+B) (C+D) = Y$$

Logic Circuit From Boolean Expression


Example:

Draw the AND-OR logic diagram for the Boolean expression: $AB + CD = Y$


Step 1: OR AB with CD

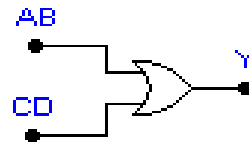

Step 2: Add top AND gate

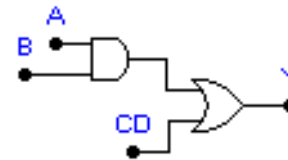

Step 3: Add bottom AND gate

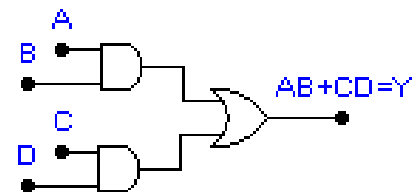





QUIZ

Draw the OR-AND logic diagram for the Boolean expression: $(A+B) \cdot (C+D) = Y$


Step 1:

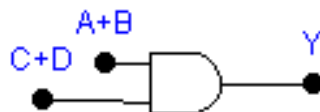

Step 2:

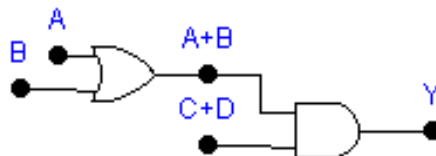

Step 3:

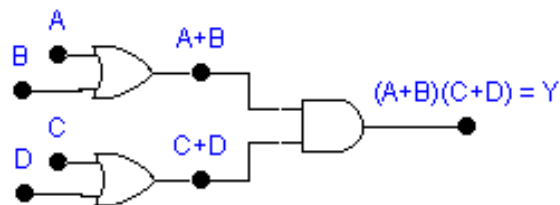

Boolean Expressions

Sum-of-products form:

$$\bar{A} \cdot B + C \cdot \bar{D} = Y$$

Also called the minterm form

Product-of-sums form:

$$(A + \bar{B}) \cdot (\bar{C} + D) = Y$$

Also called the maxterm form



QUIZ

1. The Boolean expression $AB + BC = Y$ is in _____ (product-of-sums, sum-of-products) form. **sum-of-products**
2. The Boolean expression $(A+B)(B+C) + Y$ is in _____ (product-of-sums, sum-of-products) form. **product-of-sums**
3. The Boolean expression $(A+B)(B+C) = Y$ is in _____ (maxterm, minterm) form. **maxterm**
4. The Boolean expression $AB + BC = Y$ is in _____ (maxterm, minterm) form. **minterm**

Boolean Expression from Truth Table

Write the Boolean expression that describes the logic in this truth table.

Truth Table

Input Output

ABC Y

0 0 0 0

0 0 1 0

0 1 0 1

0 1 1 0

1 0 0 0

1 0 1 0

1 1 0 0

1 1 1 1

Step 1: Focus only on the truth table lines with outputs of 1.

Step 2: AND the inputs for these two lines and logically OR the ANDed groups.

$$\bar{A} \cdot B \cdot \bar{C} + A \cdot B \cdot C = Y$$

Minterm Boolean expression: $\bar{A} B \bar{C} + A B C = Y$



QUIZ

Truth Table

Input Output
ABC Y

0 0 0	1
0 0 1	0
0 1 0	0
0 1 1	0
1 0 0	0
1 0 1	0
1 1 0	0
1 1 1	1

Write the Boolean expression that describes the logic in this truth table.

$$\overline{A} \cdot \overline{B} \cdot \overline{C} + A \cdot B \cdot C = Y$$

Minterm Boolean expression: $\overline{A} \overline{B} \overline{C} + A B C = Y$



QUIZ

Truth Table
Input Output
ABC Y

0 0 0	0
0 0 1	0
0 1 0	0
0 1 1	1
1 0 0	0
1 0 1	0
1 1 0	0
1 1 1	1

1. Write the sum-of-products Boolean expression for this truth table.

$$A'BC + ABC = Y$$

2. Write the minterm Boolean expression for this truth table.

$$A'BC + ABC = Y$$

Truth Table From Boolean Expressions

Fill in a truth table from a minterm Boolean Expression.

Minterm Boolean expression: $\bar{A} \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot B \cdot C + A \cdot B \cdot \bar{C} = Y$

Step 1: Place three 1s in output column.

Step 2: Place five 0s in blanks in output column of truth table.

Truth Table

Input	Output
ABC	Y

0 0 0	1
0 0 1	0
0 1 0	0
0 1 1	1
1 0 0	0
1 0 1	0
1 1 0	1
1 1 1	0



QUIZ

1. Fill in the output column of the truth table for the Boolean expression $A'B'C' + ABC' = Y$.

Truth Table	
Input	Output
ABC	Y
0 0 0	1
0 0 1	0
0 1 0	0
0 1 1	0
1 0 0	0
1 0 1	0
1 1 0	1
1 1 1	0

Simplifying Boolean Expressions

Truth Table
Input Output

ABC Y

0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Unsimplified Boolean Expression

$$\bar{A} \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot \bar{B} \cdot C + A \cdot \bar{B} \cdot \bar{C} + A \cdot B \cdot \bar{C} = Y$$

This line is not to be considered in the loop.

Simplified Expression: $A \cdot \bar{C} + \bar{A} \cdot \bar{B} = Y$

RULE:

Eliminate term within loop that contains a term and its complement.

Simplify Boolean Expression

(Karnaugh map method)

Unsimplified Boolean expression (3 variables):


$$A \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot \bar{B} \cdot C + A \cdot B \cdot \bar{C} = Y$$

Step 1: Plot 1s

Step 2: Loop groups

Step 3: Eliminate variables

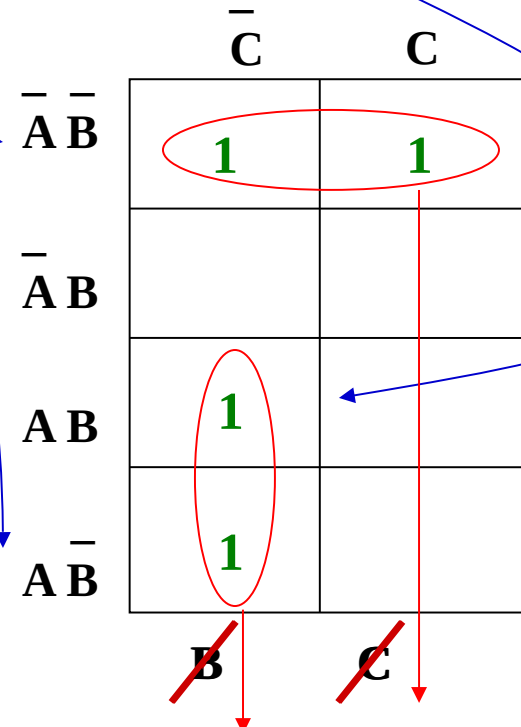Step 4: Form simplified
minterm expression



Simplified Expression: $A \bar{C} + \bar{A} \bar{B} = Y$



QUIZ

Simplify Boolean Expression (Karnaugh map method)

Unsimplified Boolean expression (4 variables):


$$\bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} = Y$$

Step 1: Plot 1s

Step 2: Loop groups

Step 3: Eliminate variables

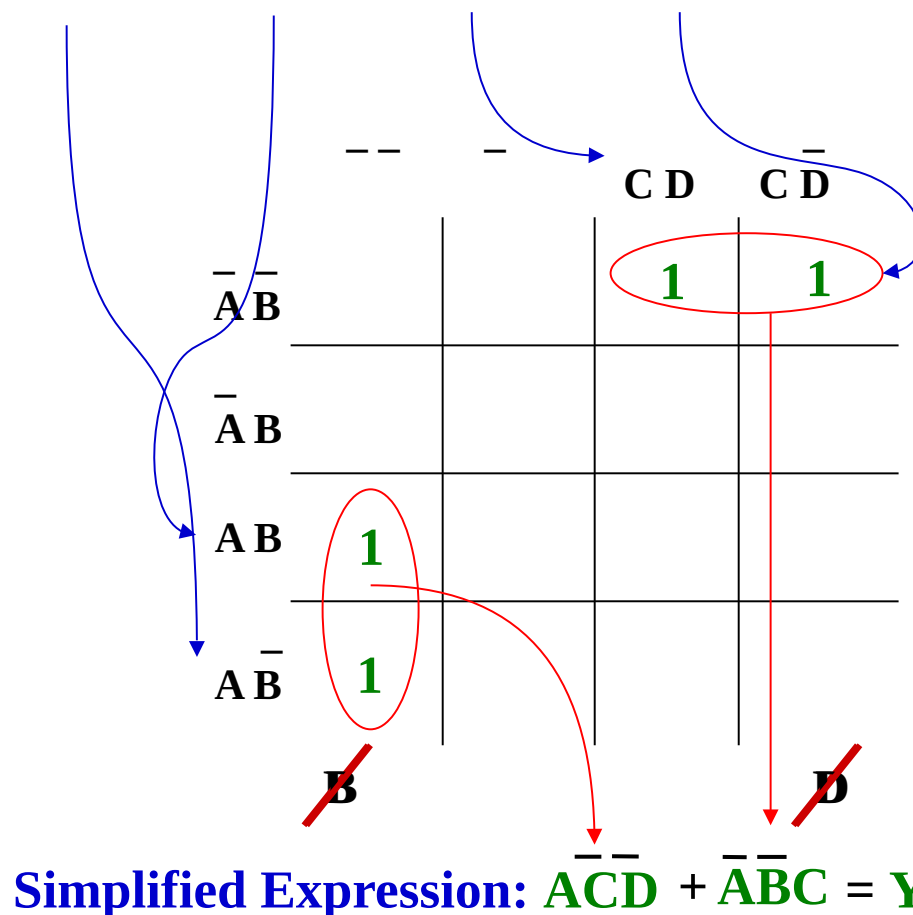
Step 4: Form simplified
minterm expression




Developing a NAND Logic Diagram

Minterm expression: $\bar{A}B + A\bar{B} = Y$

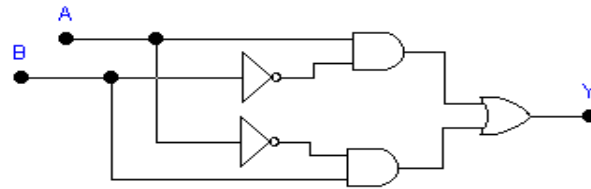Step 1: Draw AND-OR logic diagram from minterm expression.



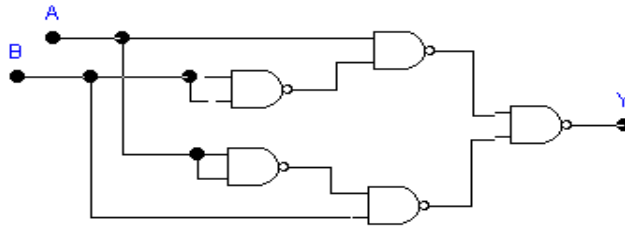Step 2: Substitute NAND gates for each inverter, AND, and OR gate.



NOTE: Both logic diagrams will generate the same truth table.

Variations in Boolean Expressions

Boolean expression (textbook style):


$$\overline{A} \overline{B} = Y$$

Boolean expression (keyboard style):


$$A' B' = Y$$



QUIZ

1. The Boolean expression $A \bar{B} + \bar{C} D = Y$ is written as _____ in keyboard style.

$$A B' + C'D = Y$$

2. The Boolean expression $\overline{A+B+C} = Y$ is written as _____ in keyboard style.

$$(A+B+C)' = Y$$

3. The Boolean expression $\bar{A} \bar{B} \bar{C} = Y$ is written as _____ in keyboard style.

$$A' B' C' = Y$$

DeMorgan's Theorems

First theorem:

$$\overline{A + B} = \bar{A} \bar{B}$$

Both used
to eliminate
long overbars


Second theorem:

$$\overline{A \bar{B}} = \bar{A} + \bar{\bar{B}}$$

DeMorgan's Theorems


First theorem:

$$\overline{A + B} = \bar{A} \bar{B}$$

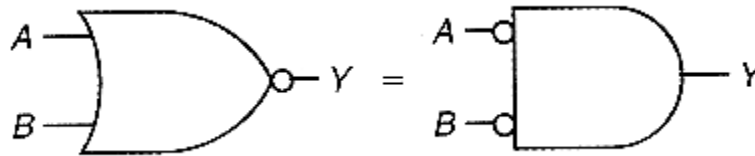

Second theorem:
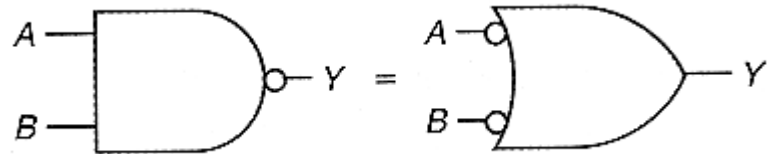
$$\overline{\bar{A} \bar{B}} = \bar{\bar{A}} + \bar{\bar{B}}$$





QUIZ

1. The statement $\overline{A \cdot B} = \overline{A} + \overline{B}$ is DeMorgan's _____ (first, second) theorem and suggests converting from a NAND to an OR situation.

second

2. The statement $\overline{A + B} = \overline{A} \cdot \overline{B}$ is DeMorgan's _____ (first, second) theorem and suggests converting from a NOR to an AND situation.

first