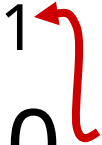


# INTRODUCTION

- *Binary Addition*
- *Half & Full Adders*
- *Parallel Adders*

# Binary Addition

- Conceptually similar to decimal addition
- *Example:* Add the binary numbers 1010 and 11

$$\begin{array}{r} \text{(carry)} \\ 1 \\ 1 \ 0 \ 1 \ 0 \\ + \quad \quad 1 \ 1 \\ \hline 1 \ 1 \ 0 \ 1 \end{array}$$




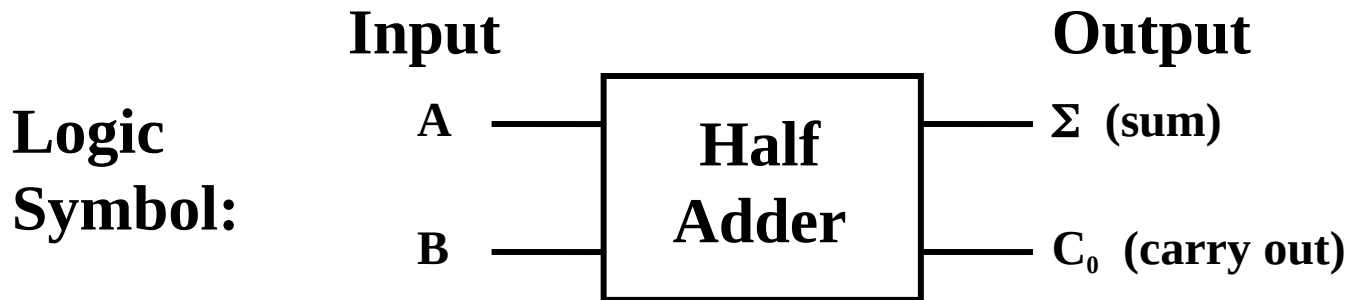
# QUIZ

**Add the Binary numbers 11010 and 1100**


$$\begin{array}{r} \text{(carry)} \text{(carry)} \\ 1 \quad 1 \\ 1 \quad 1 \quad 0 \quad 1 \quad 0 \\ + \quad 1 \quad 1 \quad 0 \quad 0 \\ \hline 1 \quad 0 \quad 0 \quad 1 \quad 1 \quad 0 \end{array}$$

# Half Adder

- Logic device that adds two binary numbers
- Only adds Least Significant Digit (LSD) column (1s column) in binary addition



Logic Diagram:

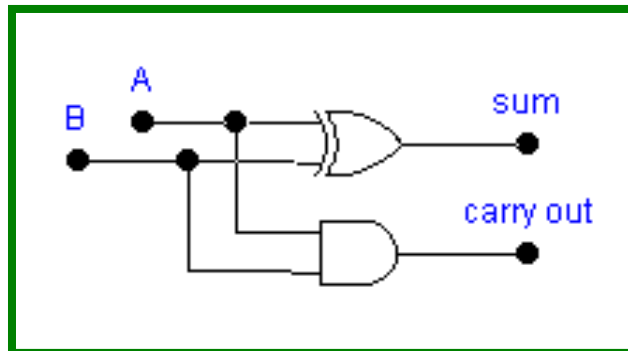




# QUIZ

**Q#5- What are the sum and carry out outputs from the half adder circuit?**

**ANS: Sum=1, Carry out=0**

**A = 1**


**B = 0**

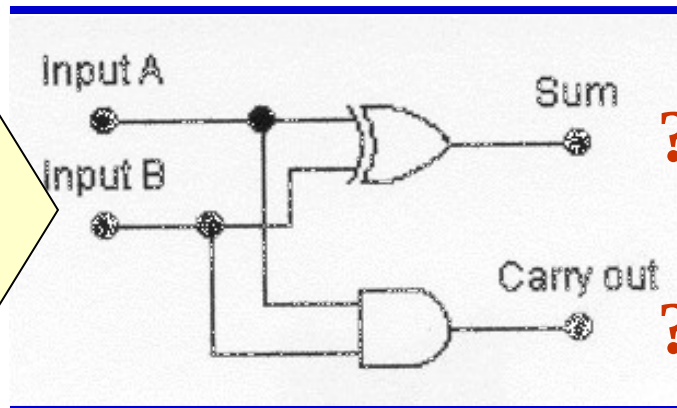


# Full Adder

Used for adding binary place values other than the 1s place

Logic  
Symbol:

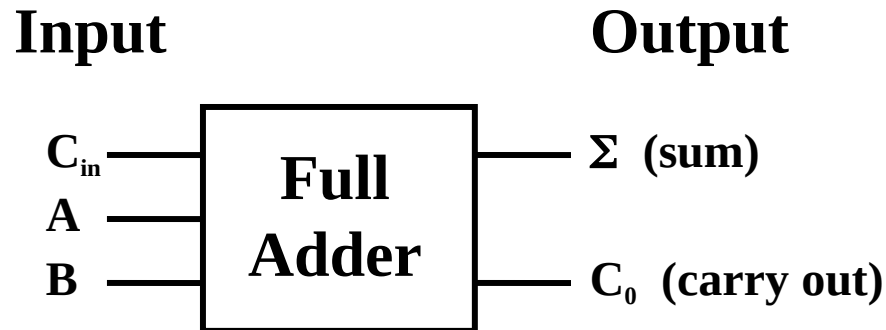

Logic  
Diagram:

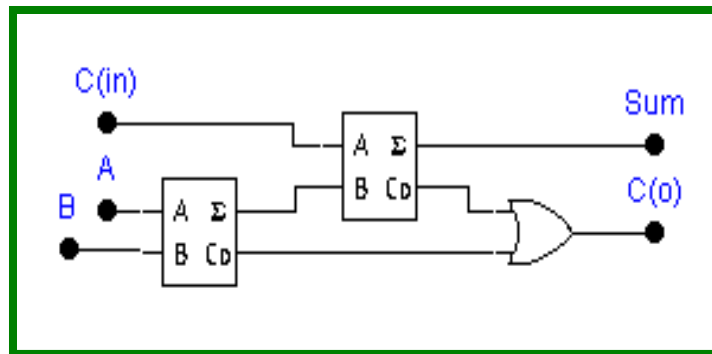



# QUIZ


**Q#6- What are the sum and carry out outputs of this full-adder circuit?**

**ANS: Sum=0, Carry out=1**

**Cin = 0**

**A = 1**


**B = 1**

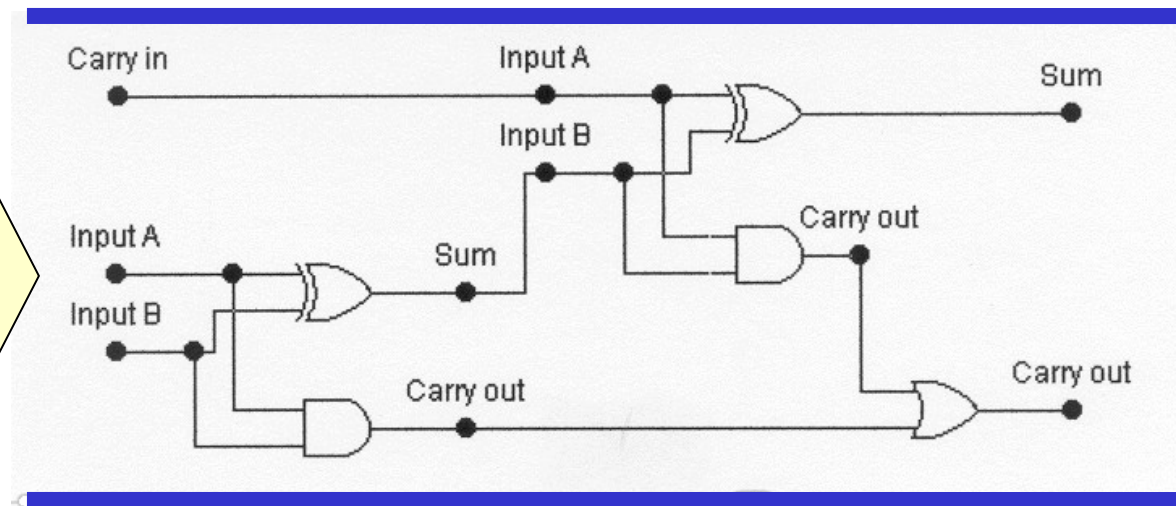
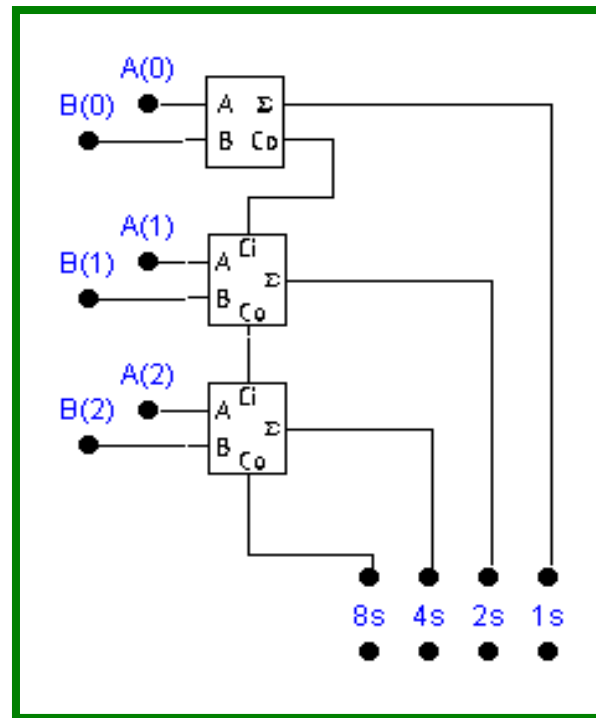
# Parallel Adding

- Use half adder for LSD
- Use full adder for other digits

$$\begin{array}{r} A_2 \quad A_1 \quad A_0 \\ + B_2 \quad B_1 \quad B_0 \\ \hline \end{array}$$






# Parallel Adder

Enter binary numbers  
to be added

1 1 1 0 + 0 1 1 0

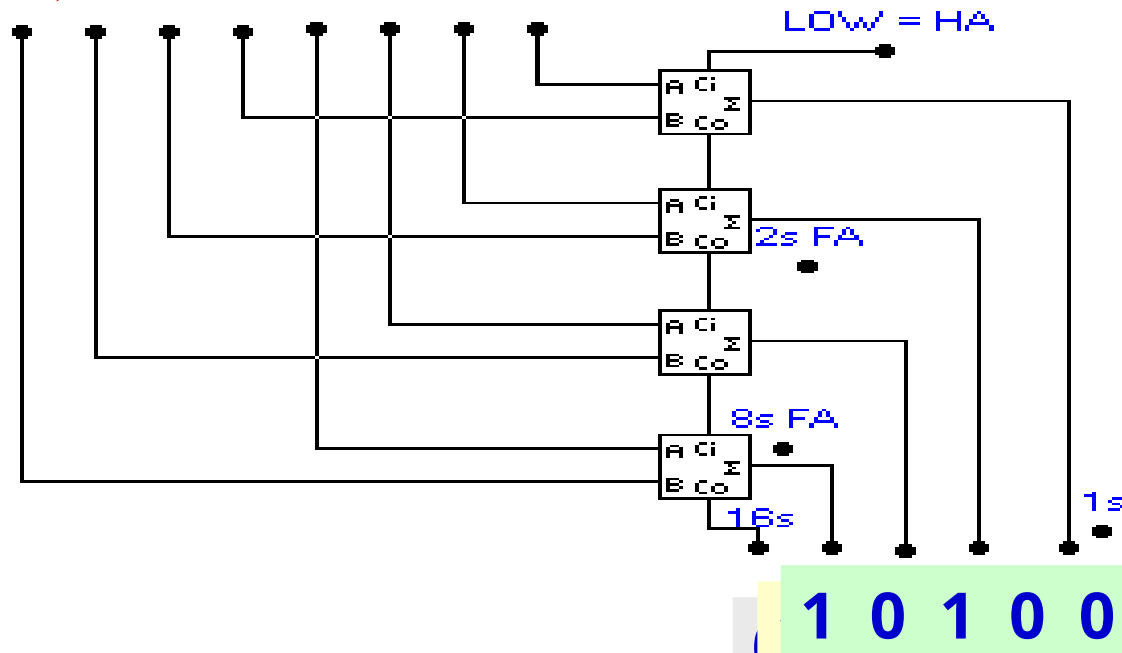

SUM appears here

Parallel adders are available in IC form.


1s place uses half-adder

2s, 4s, 8s places use full adders



# QUIZ

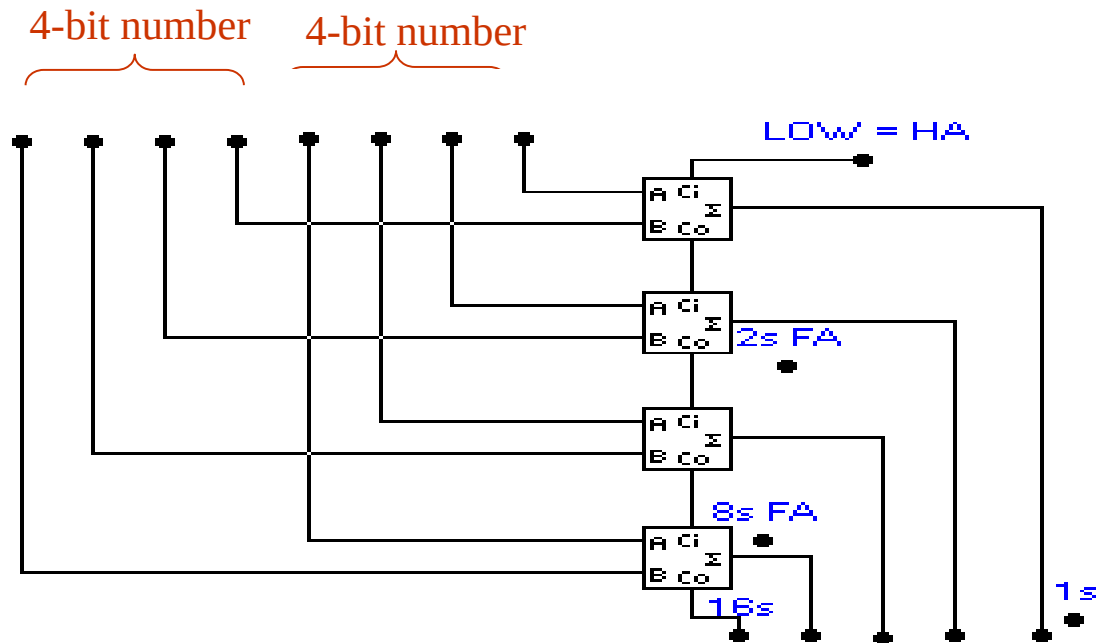**Q#7- When the 4-bit parallel adder adds binary 1010 and 1001 the sum appearing at the lower right will be \_\_\_\_.**



**ANS: 10011**