

CSEE223 Lab

Name: _____

Logic Gates

Date: _____

Reading

Lecture on the Logic Gates

Objectives

After performing this experiment, you will be able to

1. Construct a basic logic gate circuit using Multisim 2001.
2. Construct a basic logic gate circuit using a breadboard.
3. Understand the function of the 7 basic logic gates.
4. Maintain an engineering notebook during lab activities..

Materials Needed

- 1 – Windows PC with Multisim 2001
- 1 – 7408 (2-input AND gate) (OPTIONAL)
- 1 – 7432 (2-input OR gate) (OPTIONAL)
- 1 – 7400 (2-input NAND gate) (OPTIONAL)
- 1 – 7402 (2-input NOR gate) (OPTIONAL)
- 1 – 7404 (Inverter) (OPTIONAL)
- 1 – resistor 100 Ω (OPTIONAL)
- 1 – dip switch (OPTIONAL)
- 3 – LEDs (OPTIONAL)

Summary of Theory and Operation

Lecture on the Logic Gates

Procedures

1. Prelab: Complete “Logic” columns for Table1 through Table 7.
2. Use the Data Sheets and illustrations provided in pages 13 through 15 to breadboard each circuit.

3. Using Multisim/Breadboard construct the following AND Gate circuit:

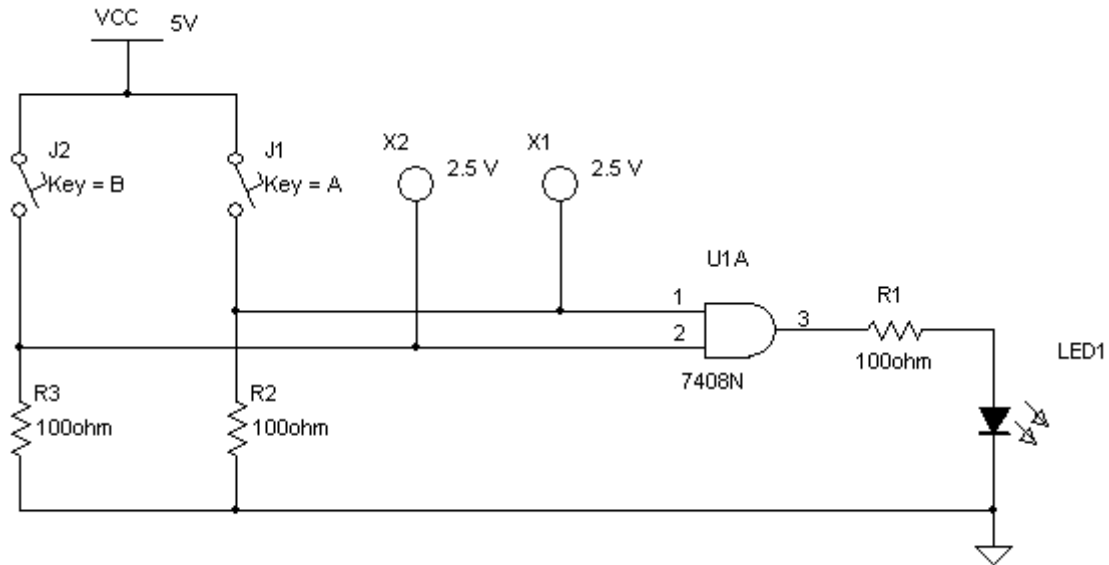


FIG 1

4. Using the A and B keys set each key to the appropriate input setting. Record the condition of the LED for each input combination. Record the logical binary equivalent at each output.

TABLE 1					
INPUTS				OUTPUT (Y)	
A		B			
X1 Lamp	Logic	X2 Lamp	Logic	LED1 (On/Off)	Logic
OFF (0V)		OFF (0V)			
OFF (0V)		ON (5V)			
ON (5V)		OFF (0V)			
ON (5V)		ON (5V)			

Prelab Signoff: _____

Breadboard Signoff: _____

Notebook Entry Signoff: _____

5. Using Multisim/Breadboard construct the following OR Gate circuit:

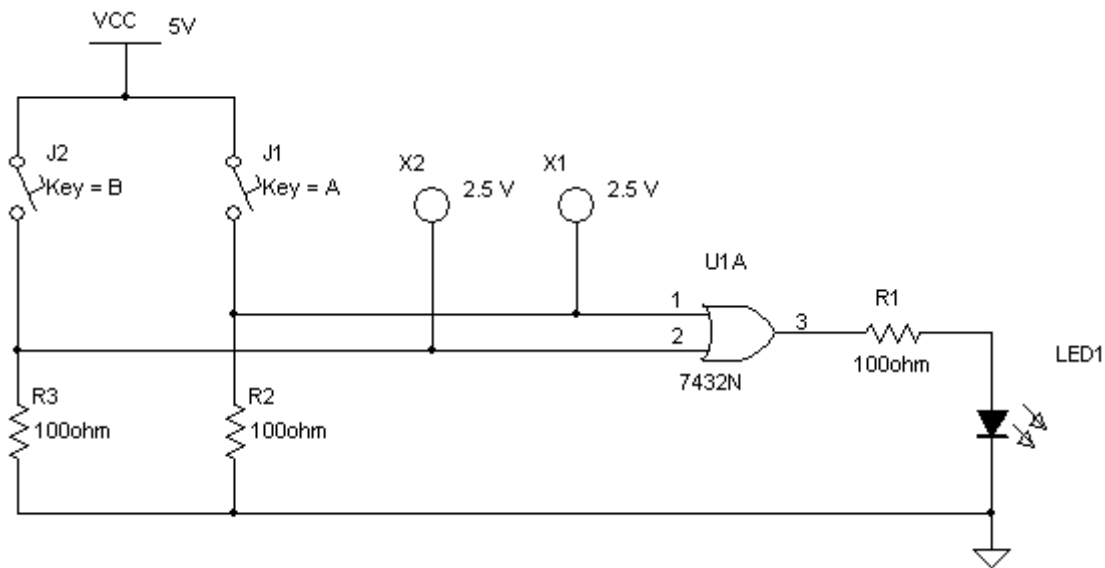


FIG 2

6. Using the A and B keys set each key to the appropriate input setting. Record the condition of the LED for each input combination. Record the logical binary equivalent at each output.

TABLE 2					
INPUTS				OUTPUT (Y)	
A		B			
X1 Lamp	Logic	X2 Lamp	Logic	LED1 (On/Off)	Logic
OFF (0V)		OFF (0V)			
OFF (0V)		ON (5V)			
ON (5V)		OFF (0V)			
ON (5V)		ON (5V)			

Prelab Signoff: _____

Breadboard Signoff: _____

Notebook Entry Signoff: _____

7. Using Multisim/Breadboard construct the following NAND Gate circuit:

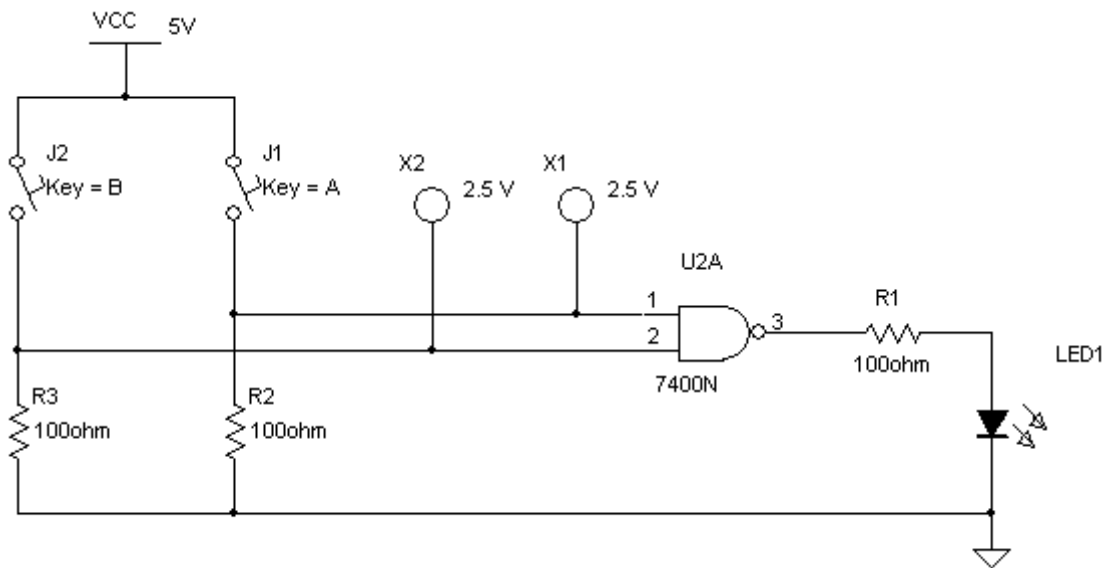


FIG 3

8. Using the A and B keys set each key to the appropriate input setting. Record the condition of the LED for each input combination. Record the logical binary equivalent at each output.

TABLE 3					
INPUTS				OUTPUT (Y)	
A		B			
X1 Lamp	Logic	X2 Lamp	Logic	LED1 (On/Off)	Logic
OFF (0V)		OFF (0V)			
OFF (0V)		ON (5V)			
ON (5V)		OFF (0V)			
ON (5V)		ON (5V)			

Prelab Signoff: _____

Breadboard Signoff: _____

Notebook Entry Signoff: _____

9. Using Multisim/Breadboard construct the following NOR Gate circuit:

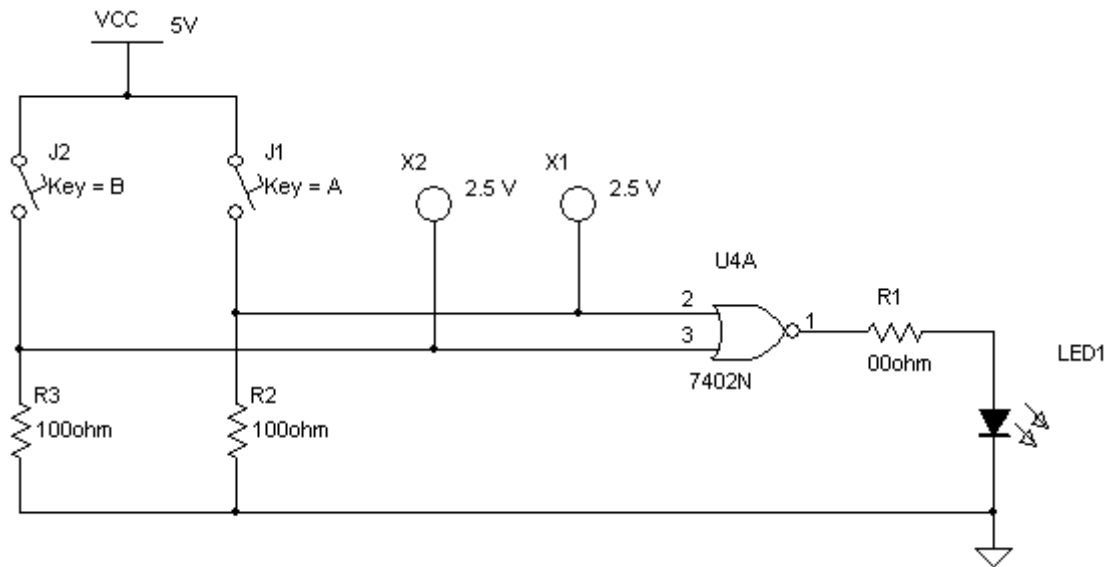


FIG 4

10. Using the A and B keys set each key to the appropriate input setting. Record the condition of the LED for each input combination. Record the logical binary equivalent at each output.

TABLE 4					
INPUTS				OUTPUT (Y)	
A		B			
X1 Lamp	Logic	X2 Lamp	Logic	LED1 (On/Off)	Logic
OFF (0V)		OFF (0V)			
OFF (0V)		ON (5V)			
ON (5V)		OFF (0V)			
ON (5V)		ON (5V)			

Prelab Signoff: _____

Breadboard Signoff: _____

Notebook Entry Signoff: _____

11. Using Multisim/Breadboard construct the following XOR Gate circuit:

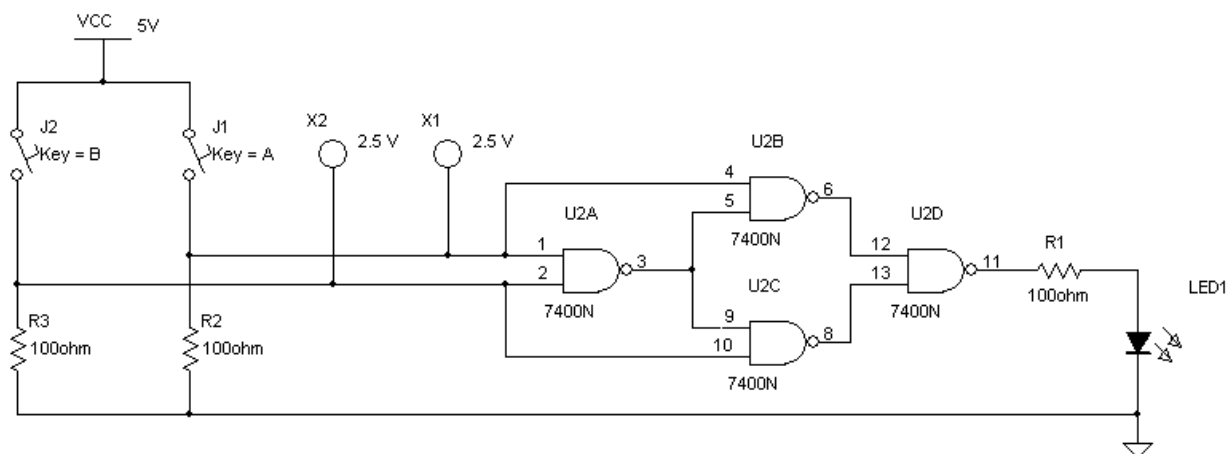


FIG 5

12. Using the A and B keys set each key to the appropriate input setting. Record the condition of the LED for each input combination. Record the logical binary equivalent at each output.

TABLE 5					
INPUTS				OUTPUT (Y)	
A		B			
X1 Lamp	Logic	X2 Lamp	Logic	LED1 (On/Off)	Logic
OFF (0V)		OFF (0V)			
OFF (0V)		ON (5V)			
ON (5V)		OFF (0V)			
ON (5V)		ON (5V)			

Prelab Signoff: _____

Breadboard Signoff: _____

Notebook Entry Signoff: _____

13. Using Multisim/Breadboard construct the following XNOR Gate circuit:

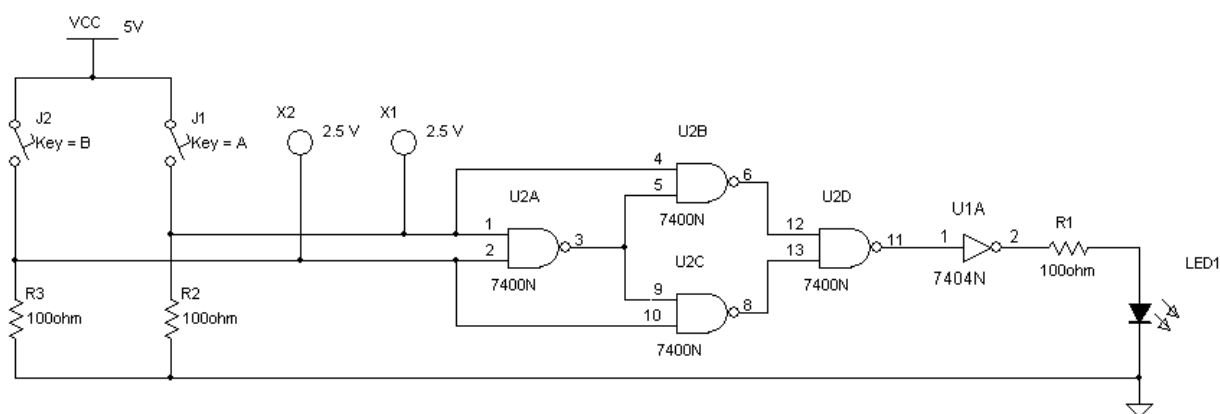


FIG 6

14. Using the A and B keys set each key to the appropriate input setting. Record the condition of the LED for each input combination. Record the logical binary equivalent at each output.


TABLE 6					
INPUTS				OUTPUT (Y)	
A		B			
X1 Lamp	Logic	X2 Lamp	Logic	LED1 (On/Off)	Logic
OFF (0V)		OFF (0V)			
OFF (0V)		ON (5V)			
ON (5V)		OFF (0V)			
ON (5V)		ON (5V)			

Prelab Signoff: _____

Breadboard Signoff: _____

Notebook Entry Signoff: _____

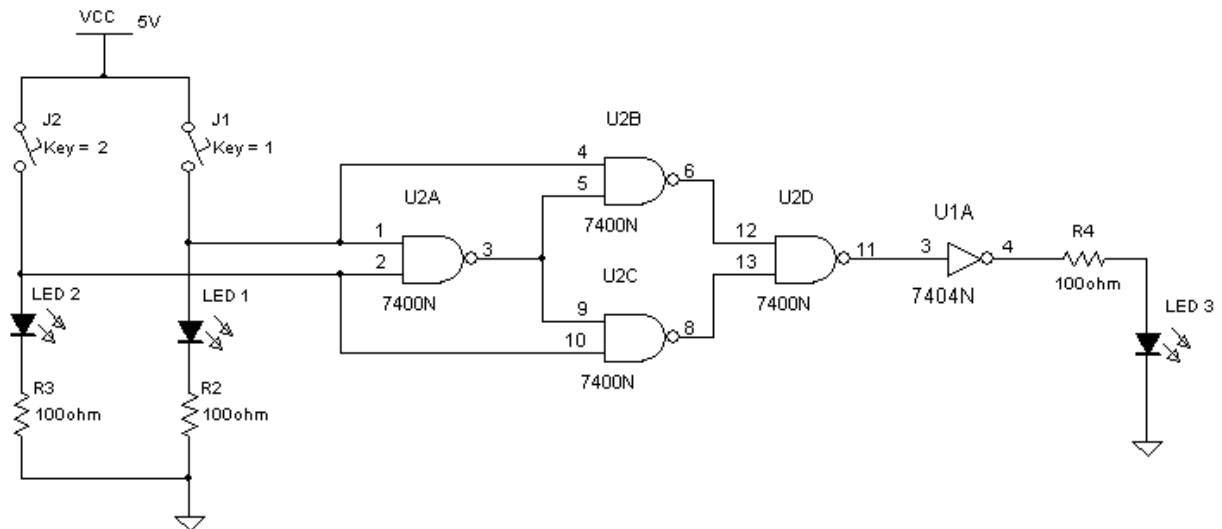15. Using the data sheets for the 7400 NAND gate IC and 7404 Invert gate IC, construct the circuit below. Connect your dip switches to the inputs of the logic and demonstrate its operation for a sign-off.



16. Using the A and B keys set each key to the appropriate input setting. Record the condition of the LED for each input combination. Record the logical binary equivalent at each output.

TABLE 7					
INPUTS				OUTPUT (Y)	
A		B			
X1 Lamp	Logic	X2 Lamp	Logic	LED1 (On/Off)	Logic
OFF (0V)		OFF (0V)			
OFF (0V)		ON (5V)			
ON (5V)		OFF (0V)			
ON (5V)		ON (5V)			

Prelab Signoff: _____

Breadboard Signoff: _____

Notebook Entry Signoff: _____

Questions

1. The AND gate is referred to as the “ALL or Nothing Gate”.
 - a. True
 - b. False
2. The XOR gate is referred to as the “Some but Not ALL” gate.
 - a. True
 - b. False
3. LOW voltage (0V) represents a
 - a. Logical 0
 - b. Logical 1
4. HIGH voltage (5V) represents a
 - a. Logical 0
 - b. Logical 1
5. A NOR gate can be constructed with an OR gate and an Inverter.
 - a. True
 - b. False
6. Write the Boolean expression for
 - a. 2-input AND gate _____
 - b. 2-input NAND gate _____
 - c. 2-input OR gate _____
 - d. 2-input NOR gate _____
7. The OR gate is referred to as the “Any or ALL” gate.
 - a. True
 - b. False
8. The NOT gate inverts or compliments the input.
 - a. True
 - b. False

9. Draw the Truth Table for a 3-input OR gate using 1's and 0's.

INPUTS			OUTPUT
A	B	C	Y

10. The NAND gate is called the Universal gate because it can be used in conjunction with any other gate to create any logic function..

- a. True
- b. False

Data Sheets




DM74LS08 Quad 2-Input AND Gates

General Description

This device contains four independent gates each of which performs the logic AND function.

Connection Diagram

 

SN5432, SN54LS32, SN54S32, SN7432, SN74LS32, SN74S32 QUADRUPL 2-INPUT POSITIVE-OR GATES


DECEMBER 1983 - REVISED MARCH 1988

description

These devices contain four independent 2-input OR gates.

The SN5432, SN54LS32 and SN54S32 are characterized for operation over the full military range of -55°C to 125°C . The SN7432, SN74LS32 and SN74S32 are characterized for operation from 0°C to 70°C .

logic diagram

 


SN5432, SN54LS32, SN54S32 . . . J OR W PACKAGE

SN7432 . . . N PACKAGE

SN74LS32, SN74S32 . . . D OR N PACKAGE

(TOP VIEW)

 


SN54LS32, SN54S32 . . . FK PACKAGE

(TOP VIEW)



QUAD 2-INPUT NAND GATE

 


SN54/74LS00
74HC00 / 74HCT00

DESCRIPTION

QUAD 2-INPUT NAND GATE
LOW POWER SCHOTTKY
OR
HIGH SPEED CMOS



QUAD 2-INPUT NOR GATE

 

SN54/74LS02

QUAD 2-INPUT NOR GATE
LOW POWER SCHOTTKY



DM74LS04 Hex Inverting Gates

General Description

This device contains six independent gates each of which performs the logic INVERT function.

Connection Diagram

