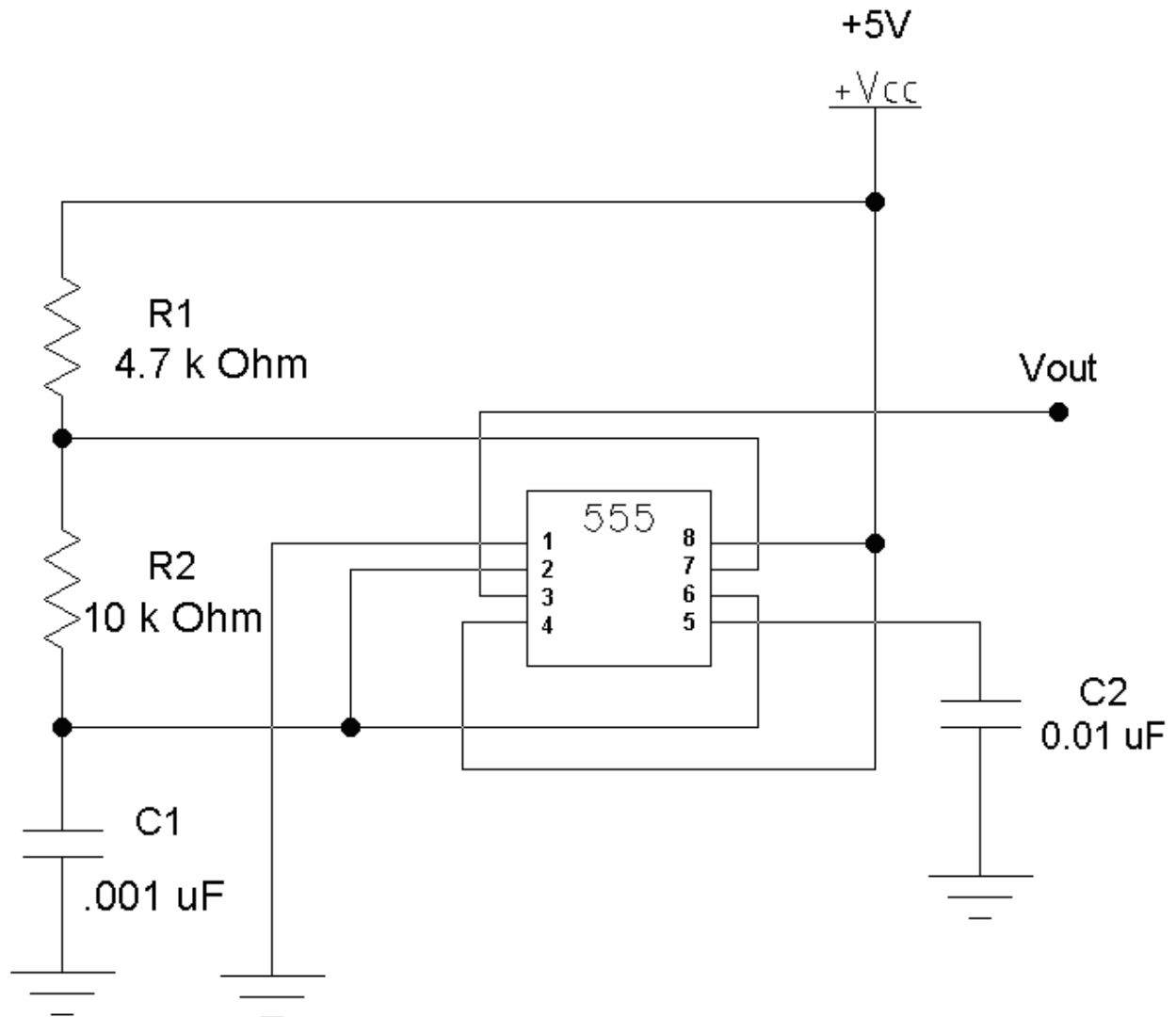



Name: _____

Multivibrator Circuits

Date:_____



1.	Circuit Type =	Astable / One Shot (circuit one)
2.	On Time =	
3.	Off Time =	
4.	Period =	
5.	Frequency =	
6.	Duty Cycle =	

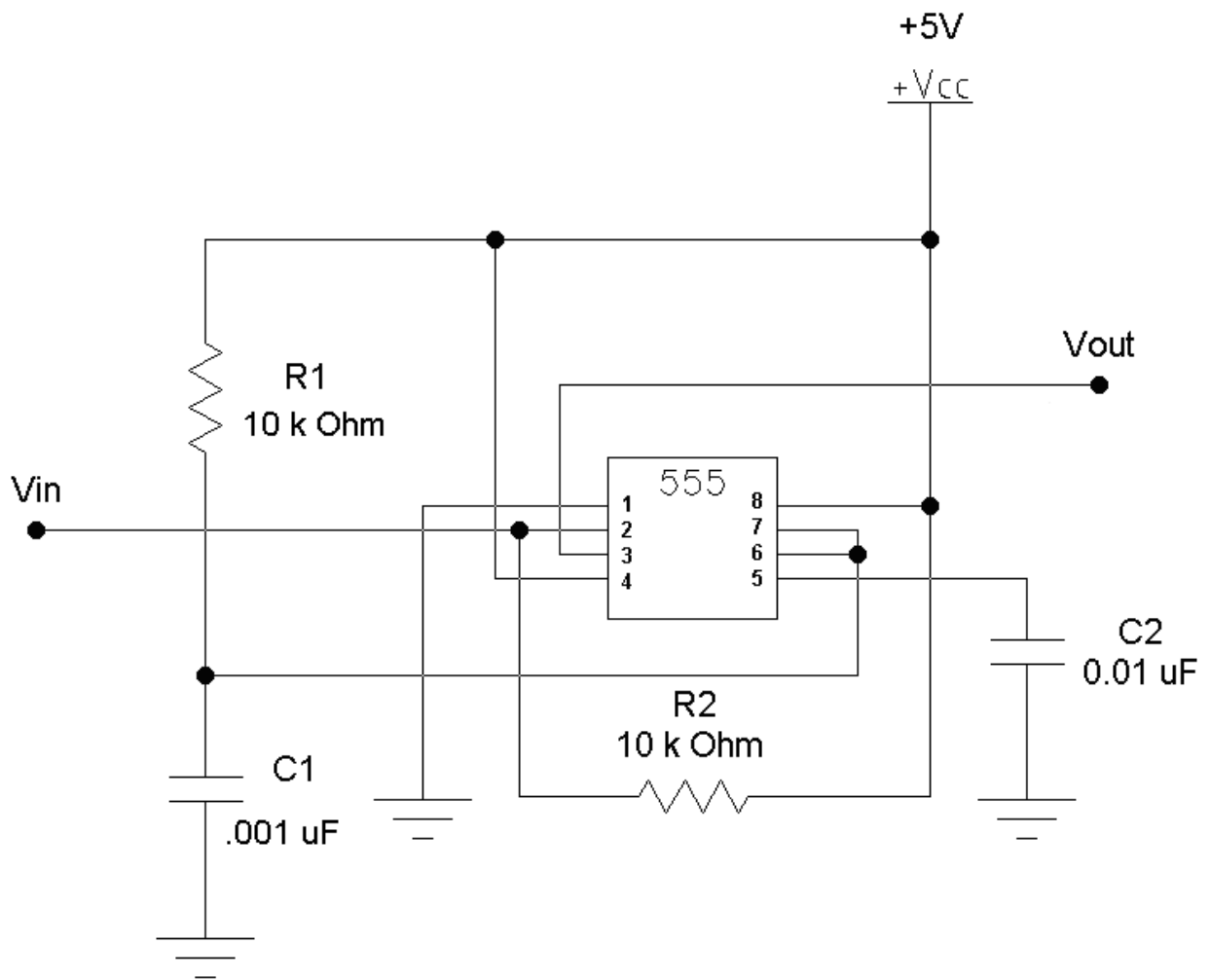

7.	Circuit Type =	Astable / One Shot (circuit one)
8.	On Time =	
9.	Off Time =	
10.	Period =	
11.	Frequency =	
12.	Duty Cycle =	

